

DAY - 13

SEAT NUMBER

--	--	--	--	--	--

2014	III	12	1100	V - 233	(E)
<b>ELECTRONICS</b> <b>PAPER - I (C-2)</b>					
Time : 3 Hours		4 Pages		Max. Marks : 50	

- Instructions :**
- (1) All questions are compulsory.
  - (2) Figures to the right indicate full marks.
  - (3) Draw neat labelled diagram wherever necessary.
  - (4) Use of log table is allowed.

1. (A) Select correct alternatives from the following sub-questions and rewrite complete sentences :
- (a) Charged Coupled Device works on \_\_\_\_\_. 1
    - (i) Inductive Effect
    - (ii) Capacitive Effect
    - (iii) Resistive Effect
    - (iv) Photo Electric Effect
  - (b) In a Monostable Multivibrator, the terminals \_\_\_\_\_ are connected directly to each other. 1
    - (i) Threshold and  $V_{cc}$
    - (ii) Threshold and Trigger
    - (iii) Threshold and Discharge
    - (iv) Reset and Trigger
  - (c) If a constant D.C. Voltage is applied as input to an integrator using OP-AMP, then the Output Voltage has \_\_\_\_\_ nature. 1
    - (i) Ramp
    - (ii) Sinusoidal
    - (iii) Cosine
    - (iv) Sawtooth


- (d) The unit of deflection sensitivity of CRT is \_\_\_\_\_ 1
- (i) mm/volt
  - (ii) volt/mm
  - (iii) cm
  - (iv) volt  $\times$  mm
- (B) Attempt **any two** of the following :
- (a) Derive an expression for Instantaneous Value of AM Wave. 3
  - (b) Mention parameters for Selection of Transducer. 3
  - (c) Explain how CRO displays a Waveform on the Screen. 3
2. (A) Attempt **any two** of the following :
- (a) Explain frequency response of OP-AMP. 3
  - (b) Compare Half Wave Rectifier, Full Wave Rectifier (Bridge), Full Wave Centre Tapped Rectifier. (Any six points) 3
  - (c) In an adjustable voltage regulator calculate range of output voltage obtained from the following data : 3
    - $R_1 = 200\Omega$
    - $R_2 = 1k\Omega - 4.7\Omega$
- (B) Attempt **any one** of the following :
- (a) Draw block diagram of FAX Machine and explain function of each block. 4
  - (b) Draw labelled diagram of CRT and explain function of each Electrode. 4
3. (A) Attempt **any two** of the following :
- (a) Explain use of OP-AMP as Inverting Adder. 3
  - (b) Explain characteristics of Zener Diode with suitable graph. 3
  - (c) Explain working of Thermistor and LDR. 3

(B) Attempt **any one** of the following :

(a) Find :

4

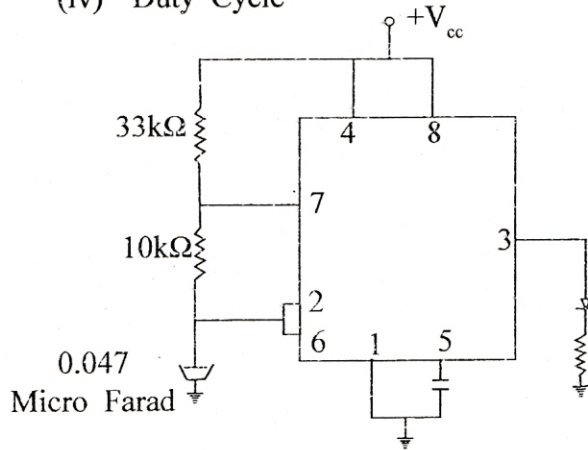- (i) Charging Time
- (ii) Discharging Time
- (iii) Frequency
- (iv) Duty Cycle



(b) Define the following terms in Frequency Modulation :

4

- (i) Frequency Deviation
- (ii) Guard Band
- (iii) Carrier Swing
- (iv) Modulation Index

4. (A) Attempt **any two** of the following :

(a) State Linear and Non-linear Applications of OP-AMP.

3

(b) Explain working of Full Wave Centre-tapped Rectifier Circuit.

3

(c) Peak-to-peak Divisions of Waveform on a CRO Screen is 4 Division and horizontally spread over 5 Divisions. If volt/div is at 5V/div and Time/div is at 2 msec/div, find Frequency and Magnitude of unknown Voltage.

3

(B) Attempt **any one** of the following :

(a) Explain use of OP-AMP as Inverting Amplifier and explain concept of Virtual Ground.

4

(b) Define Active Transducer. Explain working of Piezo Electric Crystal.

4

5. (A) Attempt **any two** of the following :
- (a) What is RADAR ? Explain Concept of Pulsed and Continuous Wave RADAR. 3
  - (b) Explain Action of Capacitor Filter. 3
  - (c) Draw Pin Configurations of : 3
    - (i) LM 317
    - (ii) LM 741
    - (iii) LM 555
- (B) Attempt **any one** of the following :
- (a) Explain working of Transistorised Series Voltage Regulator. Write expression for output voltage. 4
  - (b) Explain the following parameters of OP-AMP : 4
    - (i) Open Loop Gain
    - (ii) CMRR
    - (iii) Input Offset Current
    - (iv) Slew Rate

**OR**

5. (A) Attempt **any two** of the following :
- (a) Explain different types of Communication Systems. 3
  - (b) Define Amplitude Modulation and explain it graphically. 3
  - (c) In Non-inverting Amplifier :  $R_f = 20 \text{ k}\Omega$ ,  $V_o = 3\text{V}$  for  $V_{\text{input}} = 1\text{V}$ . Find Input Resistance. 3
- (B) Attempt **any one** of the following :
- (a) Draw block diagram of OP-AMP and explain function of each block. 4
  - (b) Explain working of Zener Regulator. 4